

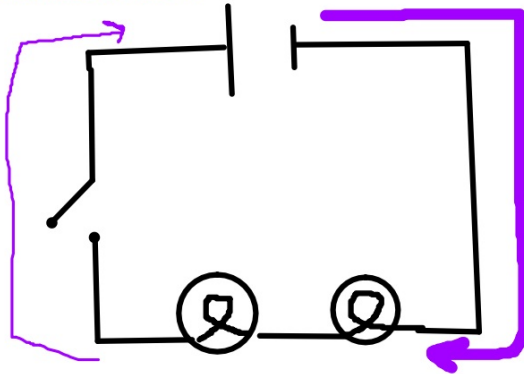


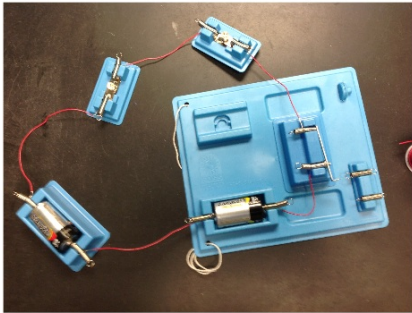How can you get two bulbs
to light at the same time?



Components in a series circuit “share” the electric energy. Cells in a series must be oriented in the same direction.

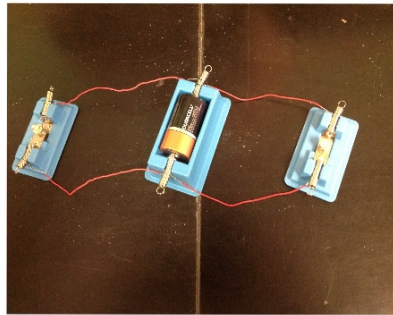How can you light two bulbs brightly with one D-cell?



A parallel circuit can run two light bulbs brightly because each have a direct pathway to the energy source. A single D-cell can run many components when they are connected in a parallel circuit.

Parallel Circuit

